
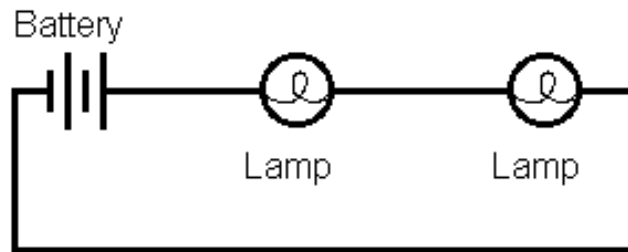


CIRCUITS:

SERIES

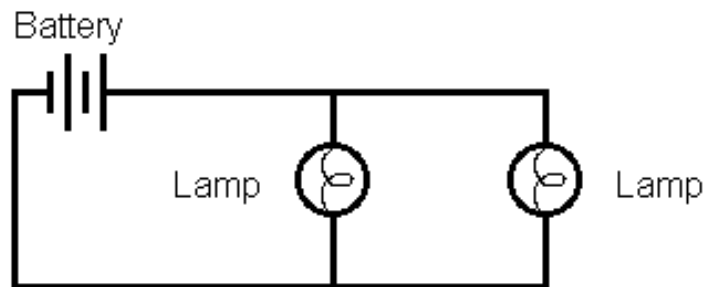

PARALLEL



Series
Vs.
Parallel

OUTCOME QUESTION(S):


S1-3-17:

What are the similarities and differences between series and parallel circuits?

Vocabulary & Concepts

Three key statements of electric circuits:

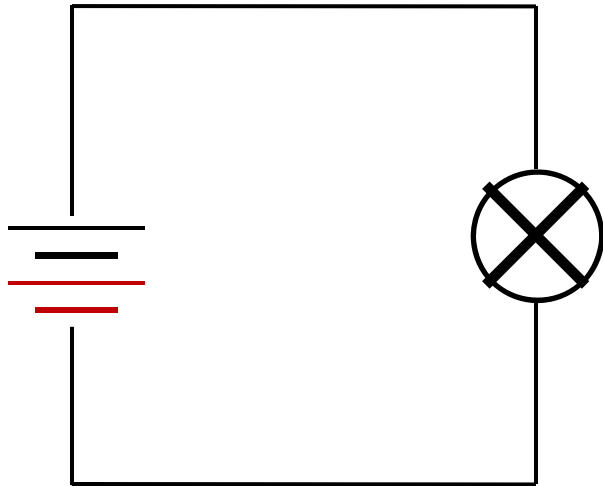
1. Voltage and current are **directly** related.
2. Voltage and resistance are **directly** related.
3. Current and resistance are **inversely** related



more energy (↑ voltage)
+ same obstacles *same resistance*
—
move faster (↑ current)

The opposite is true: **less energy** (↓ voltage) will mean **less speed** (↓ current) for the electrons

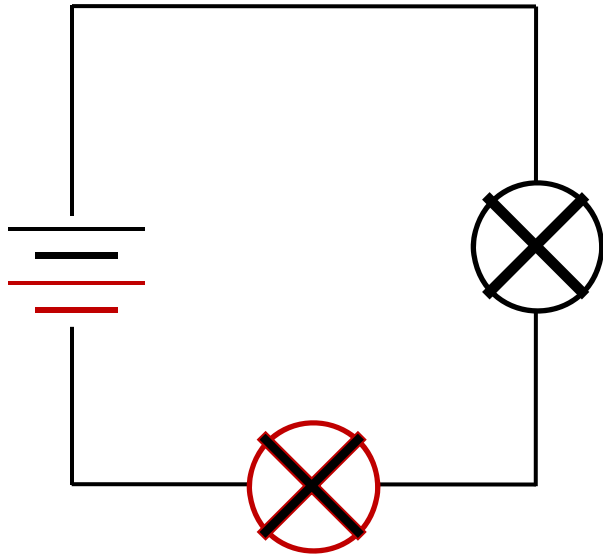
2. Voltage and resistance are **directly** related.



more obstacles (↑ resistance)
+ same speed same current
more energy (↑ voltage)

The opposite is true: **less obstacles (↓ resistance)** requires
less energy (↓ voltage) from the electrons

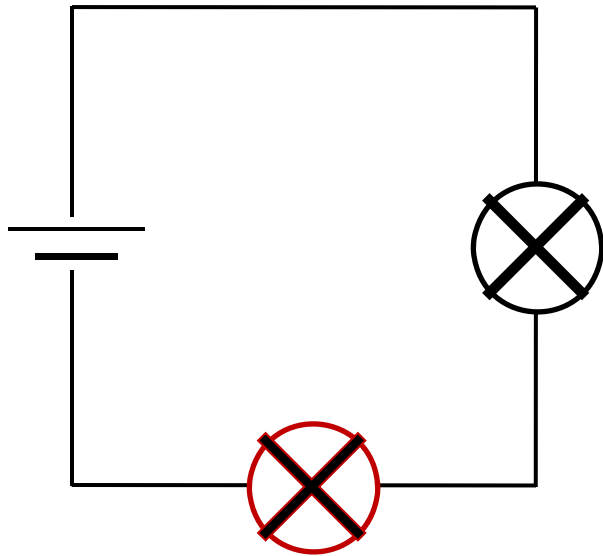3. Current and resistance are inversely related.



$$R = \frac{V}{I}$$




more obstacles (↑ resistance)
+ same energy *same voltage*
less speed (↓ current)

The opposite is true: **less obstacles** (↓ resistance) will mean **more speed** (↑ current) for the electrons

Series circuit: *one path*

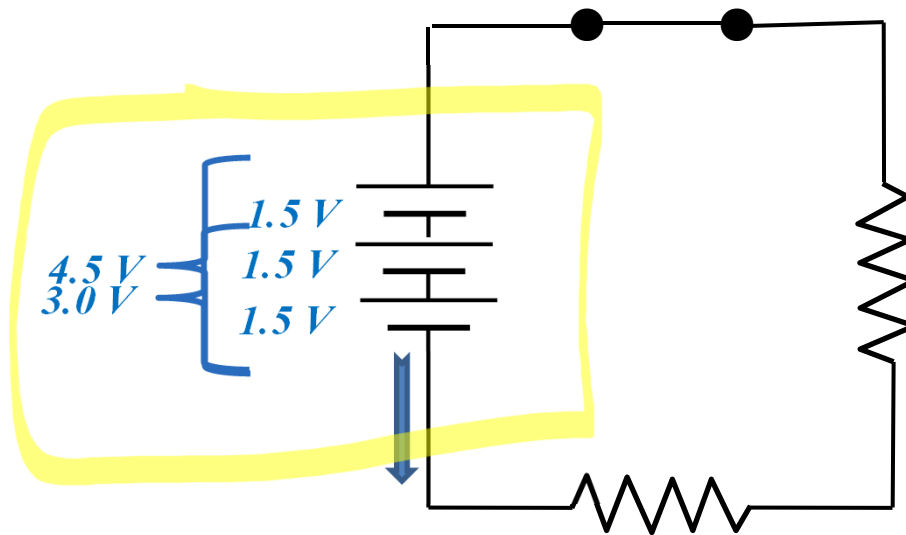
Electrons pushed through all cells in series – add them up



Total *potential* (voltage) of the electrons is the *sum* of the *cells* in *series*

Series circuit: one path

Series Connection of Light Bulbs

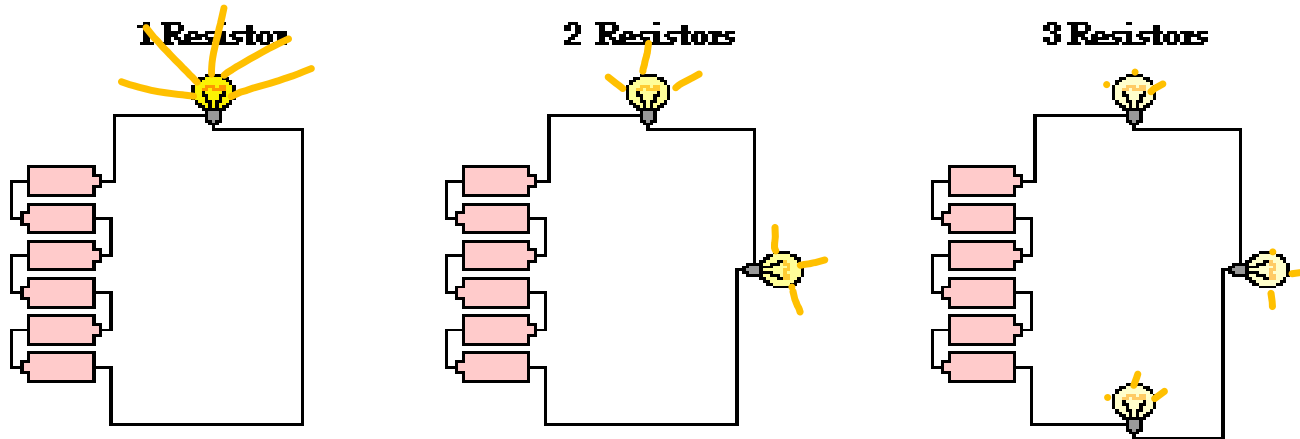


Overall current in the circuit decreases
as more resistors are added in series

Bulbs get dimmer - more resistance will mean less
current and less energy per second to the bulbs

Series circuit: *one path*


Electrons move at constant speed - measured anywhere

Current is the same at
any point

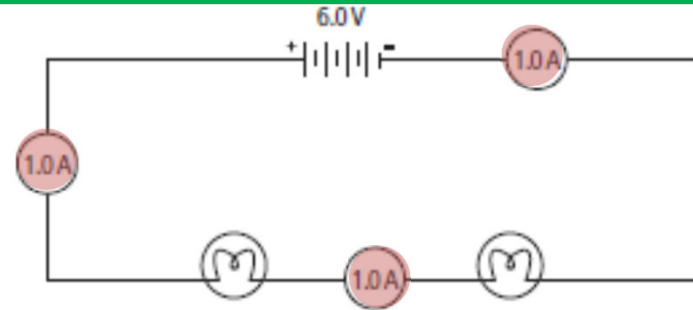

Different resistors take different amounts of energy to get past

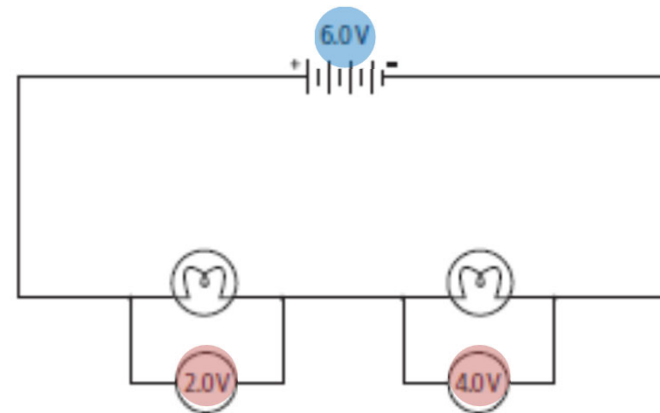
Sum of voltage drop
by all components
equals total voltage
supplied by source



Parallel circuit: *multiple pathways*

Electrons pushed through *only one* branch – energy of one

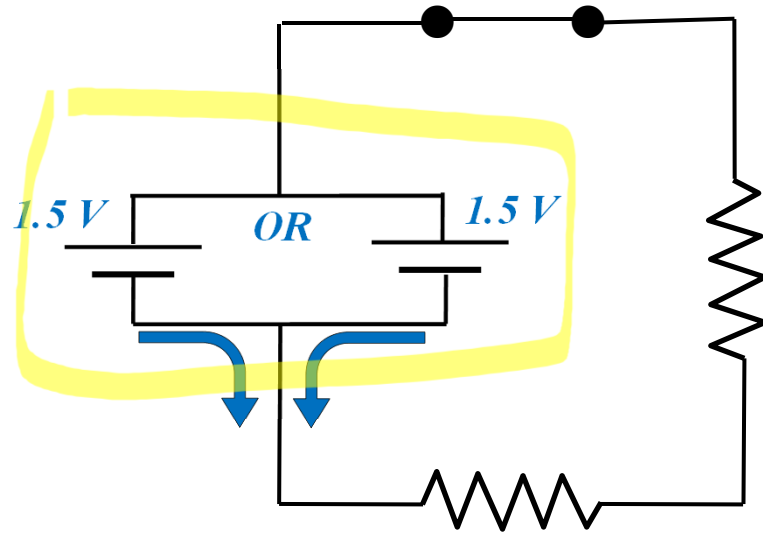
*Since cells are
splitting current of
the circuit, each cell
lasts longer*



Total *potential* of the electrons is the voltage of a single branch in parallel

Parallel circuit: *multiple pathways*

Parallel Connection of Light Bulbs

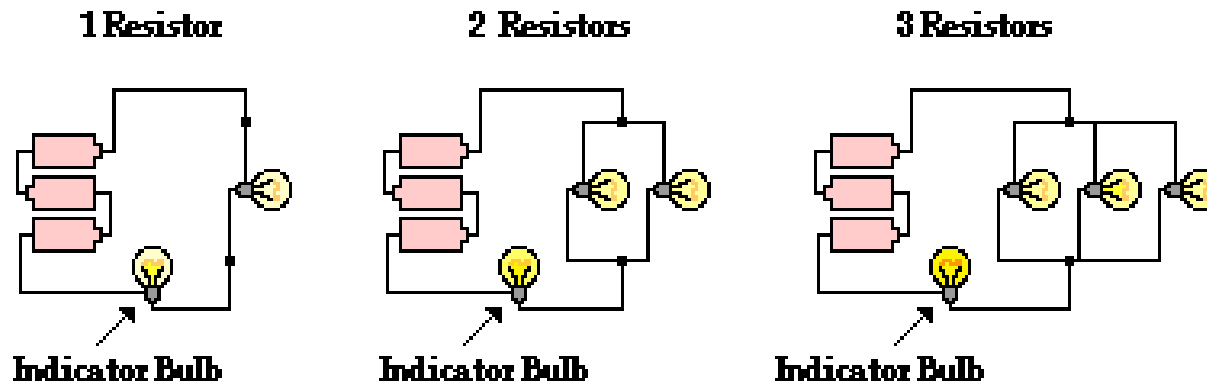


Overall current in the circuit increases
as more resistors are added in parallel

Bulbs get brighter: **more junctions** (pathways) **increases current** which means *more energy per second* to the bulbs

Parallel circuit: *multiple pathways*


Electrons move quickest through the weakest resistors

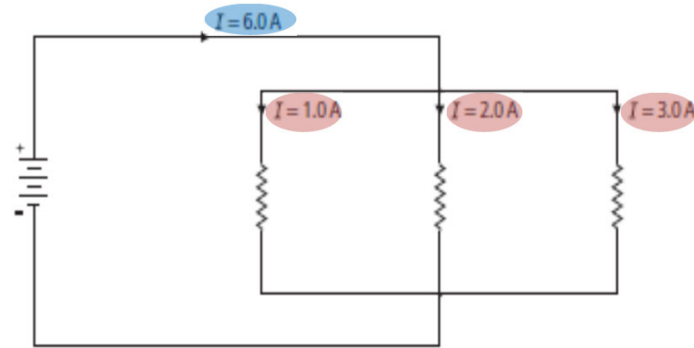Sum of all branches equals total current at the junction



Electrons **lose all** energy through circuit – regardless of path

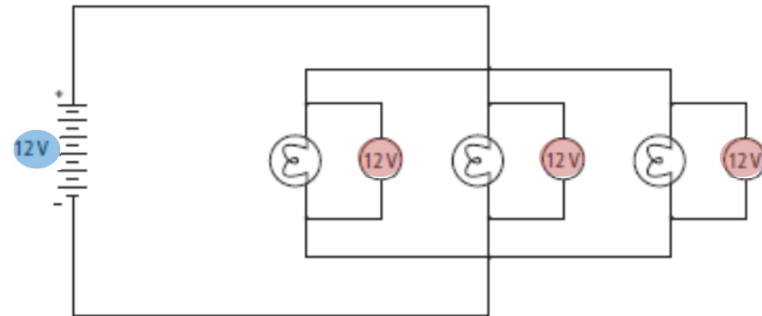Voltage drop in each branch is the same as total voltage supplied by the source



| SERIES | PARALLEL |
|---|---|
| <u>One</u> path | <u>Multiple</u> paths |
| <u>Removing</u> a component kills circuit | Current flows in other <u>branches</u> if one is broken |
| <div data-bbox="583 636 1558 706" data-label="Text"> <p><i>* BATTERIES ONLY *</i></p> </div> Total <u>voltage</u> is sum ALL cells | <u>Voltage</u> is same as single branch <i>(but it lasts longer)</i> |
| Sum of <u>voltage drop</u> by ALL components equals the total voltage supplied by source | Voltage drop in <u>EACH</u> branch equals the total voltage supplied by the source |
| Total <u>current</u> is the same at any point | Total <u>current</u> before or after the junction is the sum of current in all branches |

What will happen to the current in the circuit below for each case:

a) the switch is closed


Main current flowing - All bulbs will be “on”

b) the switch is closed and bulb 1 is removed

Main current cut - all bulbs will be “off”

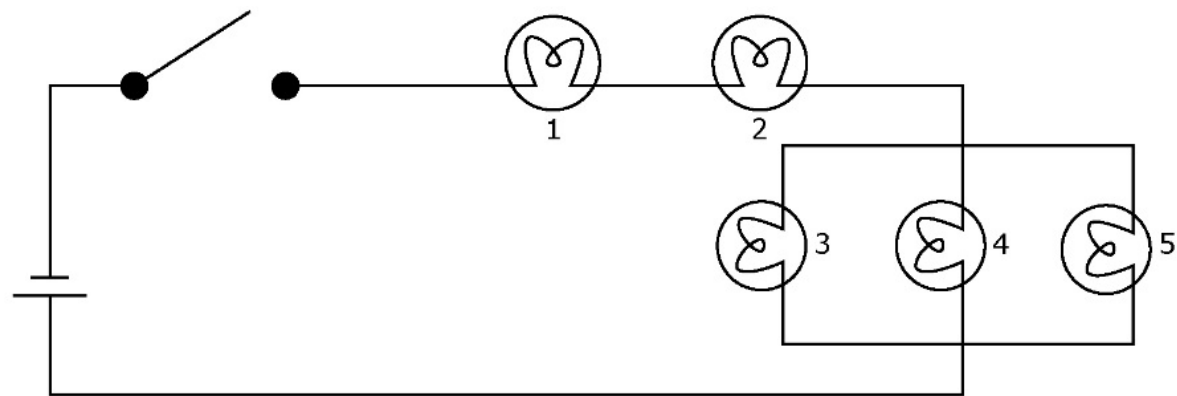c) the switch is closed and bulb 5 is removed


Current cut in branch 5 only - 1,2,3,4 will be “on”



Find the unknown voltage, V and current, A:


$$\text{Current} = 2.0 + 4.0 = 6.0 \text{ A}$$

$$\text{Voltage} = 12 \text{ V}$$

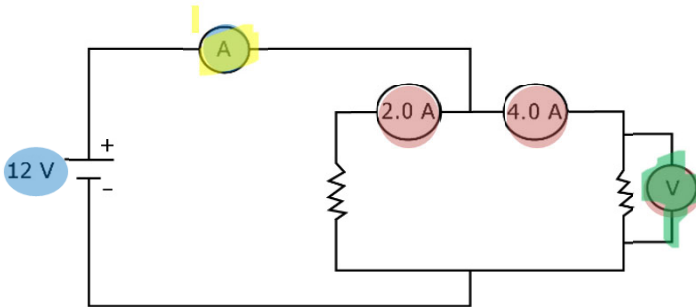

$$\text{Current} = 8.0 - 5.0 - 2.0 = 1.0 \text{ A}$$

$$\text{Voltage} = 90 \text{ V}$$

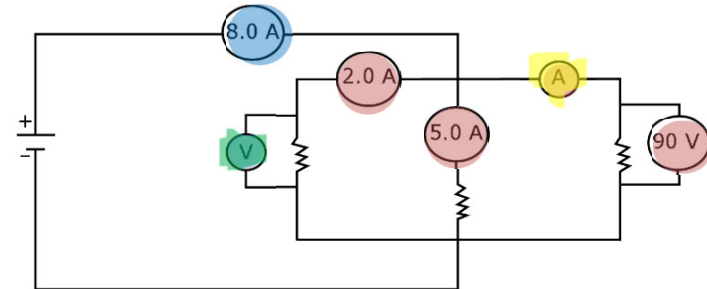

Sum of all **branches equals** total **current** at the junction

Drop in each *branch same* as total voltage supplied by the **source**

CAN YOU ANSWER THESE QUESTIONS?

S1-3-17:

What are the similarities and differences between series and parallel circuits?

Vocabulary & Concepts